

ENTIC-lab

Answers to WP questions

Igor Yuziv
Gabriel
Oriol
Albert Tomas
Daniel Vilardell

2020

Question 3.1: Which pressure increase will be observed at 3 m depth?

$$0.986 \cdot \frac{3}{10} = 0.2958 \text{Atm}$$

Question 3.2: Will this pressure depend or not on the atmospheric pressure at water surface? Why?

If what we want is to calculate the real pressure that will be exerted on the ROUV, we must also take into account the atmospheric pressure on the surface. On the other hand, if what we want is only to calculate the increase with respect of this, it will not be necessary.

Question 3.3: Analyse the circuit of Fig. 4.2 and obtain the output voltage VS. Then, find the dependence of VS on the relative variation due to deformation (x) and on the power supply voltage (V).

$$\begin{aligned} \frac{V - V_1}{R_o(1+x)} &= \frac{V_1}{R_0(1-x)} & \frac{V - V_1}{(1+x)} &= \frac{V_1}{(1-x)} \\ \frac{V - V_2}{R_o(1-x)} &= \frac{V_2}{R_o(1+x)} & \frac{V - V_2}{(1-x)} &= \frac{V_2}{(1+x)} \\ (V - V_1)(1-x) &= V_1(1+x) \\ (V - V_2)(1+x) &= V_2(1-x) \end{aligned}$$

Now we isolate V_1 and V_2 :

$$\begin{aligned} V_1 &= \frac{V(1-x)}{2} & V_2 &= \frac{V(1+x)}{2} \\ V_s &= V_2 - V_1 \text{ so } V_s = -V \cdot x \end{aligned}$$

Question 3.4: The datasheet of the sensor is available in Atenea. Identify there the full scale output, and then deduce the sensor sensitivity and its value when the supply voltage is not 10 V but 5 V.

Sensor sensitivity is $O = V \cdot P$. So when we have 2 voltages $O_1 = V_1 \cdot P$ and $O_2 = V_2 \cdot P$

We consider the same P for both inputs

$$\frac{V_1}{V_2} = \frac{O_1}{O_2}$$

$$O_2 = \frac{O_1 \cdot V_2}{V_1} = \frac{5 \cdot 0,410}{10} = 0,2V$$

Question 3.5: What output voltages V0 will provide the sensor at the water surface (at P=100 kPa) and at 3 m depth?

$$V_s = O \cdot P = 0,2 \cdot 100k = 20mV$$

$$V_{3m} = 0,2 \cdot 130k = 26mV$$

Question 3.6: In a real case and due to changing atmospheric conditions, the pressure at the water surface can be different than 100 kPa, discuss how you could fix such effect and obtain the correct pressure data.

To solve this problem, we are going to measure the atmospheric pressure in the laboratory so that we avoid errors.

Question 3.7: Analyse the circuit of Fig. 4.4 and obtain its gain expression $V_0/(V_2-V_1)$ when $R_1/R_2=R_4/R_3$. Identify the role of Rg as a gain trimmer without compromising the R1-R4 resistance matching.

$$\begin{aligned} V_1 \cdot G_1 + (V_1 - V_2) \cdot G_g + (V_1 - V_x) &= 0 \\ (V_2 - V_x) \cdot G_3 + (V_2 - V_1) \cdot G_g + (V_2 - V_o) \cdot G_4 &= 0 \\ (V_2 \cdot G_3 \cdot G_g) - V_1 \cdot G_3 \cdot (G_1 + G_2 + G_g) &= \\ = (V_o \cdot G_2 \cdot G_4) + (V_1 \cdot G_g \cdot G_2) - G_2 \cdot V_2 \cdot (G_3 + G_4 + G_g) \end{aligned}$$

Let's assume $G_2 \cdot G_4 = G_1 \cdot G_3$, then we isolate:

$$V_0 = \frac{V_2 - V_1 \cdot (G_3 \cdot G_g + G_2 \cdot G_3 + G_2 \cdot G_g + G_4 \cdot G_2)}{G_2 \cdot G_4}$$

$$\frac{V_0}{V_2 - V_1} = 1 + \frac{R_1 - R_4}{R_g} + \frac{R_4}{R_3}$$

Question 3.8: Compare this result with the gain expression provided by the manufacturer using the resistor values shown in the INA126 datasheet.

$$G = 5 + \frac{80k\Omega}{R_g}$$

$$R_4 = R_1 = 40k\Omega \quad R_2 = R_3 = 10k\Omega$$

Question 3.9: Identify the saturation voltage of the amplifier

$$5V - 0,75V = 4,25V = V_{sat}$$

Question 3.10: Which amplifier gain is necessary to obtain the maximum amplifier voltage output for 3m depth? Which R_g resistor value will provide this gain?

$$G = \frac{v_{sat}}{v_{in}} = \frac{4.25}{26} = 163.46$$

$$R_g = \frac{80}{163.46 - 5} = 504.86 \Omega \approx 510 \Omega$$


Question 3.11: Draw the sensor+amplifier schematic using the CAD schematic software <https://www.tinycad.net/>


FALTA ESQUEMA

Question 3.12: Obtain in the lab 10 measurement points along the measurement range. Draw its graphical representation, calculate and plot the linear regression and the linearity error (lineal regression straight line – measured points).

Preassure[Atm]	Voltage[V]
0	1.96
0.1	1.97
0.15	1.98
0.2	1.99
0.25	1.995
0.3	2.00
0.35	2.003
0.4	2.01
0.45	2.013
0.5	2.019

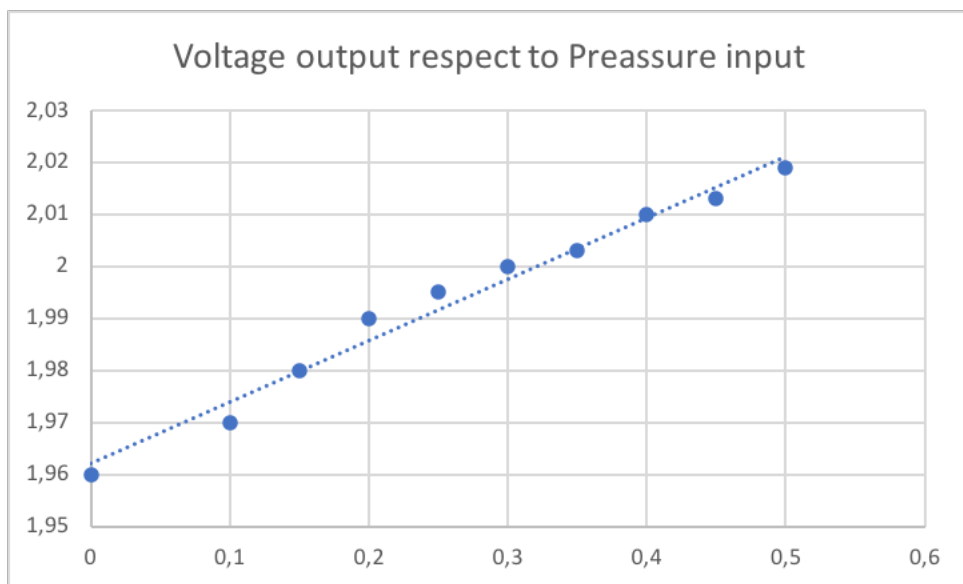Taula 1: Voltage output respect to Preassure input



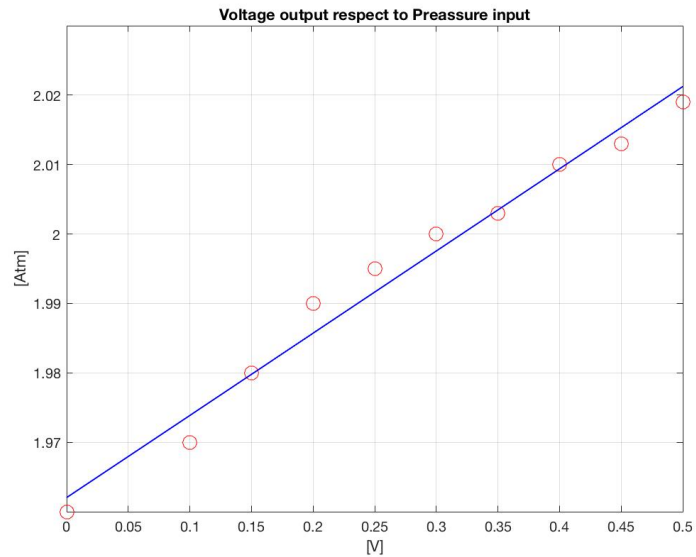

```

1 clear;
2 x = [ 0; 0.1; 0.15; 0.2; 0.25; 0.3; 0.35; 0.4; 0.45;
      0.5];
3 y = [1.96; 1.97; 1.98; 1.99; 1.995; 2.00; 2.003; 2.01;
      2.013; 2.019]
4
5 plot(x, y, 'ro', 'MarkerSize', 10);
6 grid on;
7 % Get the fit
8 coeffs = polyfit(x, y, 1);
9 % Get the x values for the fit at higher resolution.
10 xFit = linspace(x(1), x(end), 300);
11 % Get the estimated y values
12 yFit = polyval(coeffs, xFit);
13 % Plot them as a line.
14 hold on;
15 xlabel(' [V] ')
16 ylabel(' [Atm] ')
17 title(' Voltage output respect to Preassure input ')
18 plot(xFit, yFit, 'b-', 'LineWidth', 1);

```

Question 3.13: Calculate the digital data range provided by the acquisition circuit in measurements from 0 to 3m of water depth. Consider that the 10 bit A/D converter of the Arduino assigns 0 to a 0V input and 1023 (2¹⁰-1) to a 5V input.

The expected values from the arduino measurement acquisition should be inside the interval

$$\left[\frac{V_0}{5} \cdot 1023, \frac{V_{0.3}}{5} \cdot 1023\right] = \left[\frac{1.96}{5} \cdot 1023, \frac{2.00}{5} \cdot 1023\right] = [401.0, 409.2]$$

Question 3.14: Explain briefly what is the purpose of the following functions, used in the sketch of Fig. 4.5: `Serial.begin()`, `analogRead()`, `Serial.println()` and `delay()`.

- **`Serial.begin()`:** Sets the data rate in bits per second for serial data transmission.
- **`analogRead()`:** Reads the value from the specified analog pin.
- **`Serial.println()`:** Prints data to the serial port and skip the line.
- **`delay()`:** Pauses the program for the amount of time specified as parameter.

Question 3.15: While acquiring measures with the Arduino, smoothly increase the pressure to simulate a depth change from 0 m to 3 m. Do the measurement results displayed on the serial monitor match with the theoretical ones obtained in Question 3.13? If not, explain why. NOTE: If you are at home, use the potentiometer or the temperature sensor instead of the pressure sensor.

Preassure[Atm]	Arduino output
0	391
0.1	392
0.15	392
0.2	393
0.25	394
0.3	395
0.35	396
0.4	397
0.45	399
0.5	399

Taula 2: Arduino output respect to Preassure input

FALTA EXPLICAR PERQUE NO ES IGUAL A LA PREGUNTA 3.13

Question 3.16: Include a picture of the initial and final Gantt diagrams of WP3, making a reflexion about the progress and explaining any delay in the development of the tasks.

ES FA AL ACABAR LA PART